
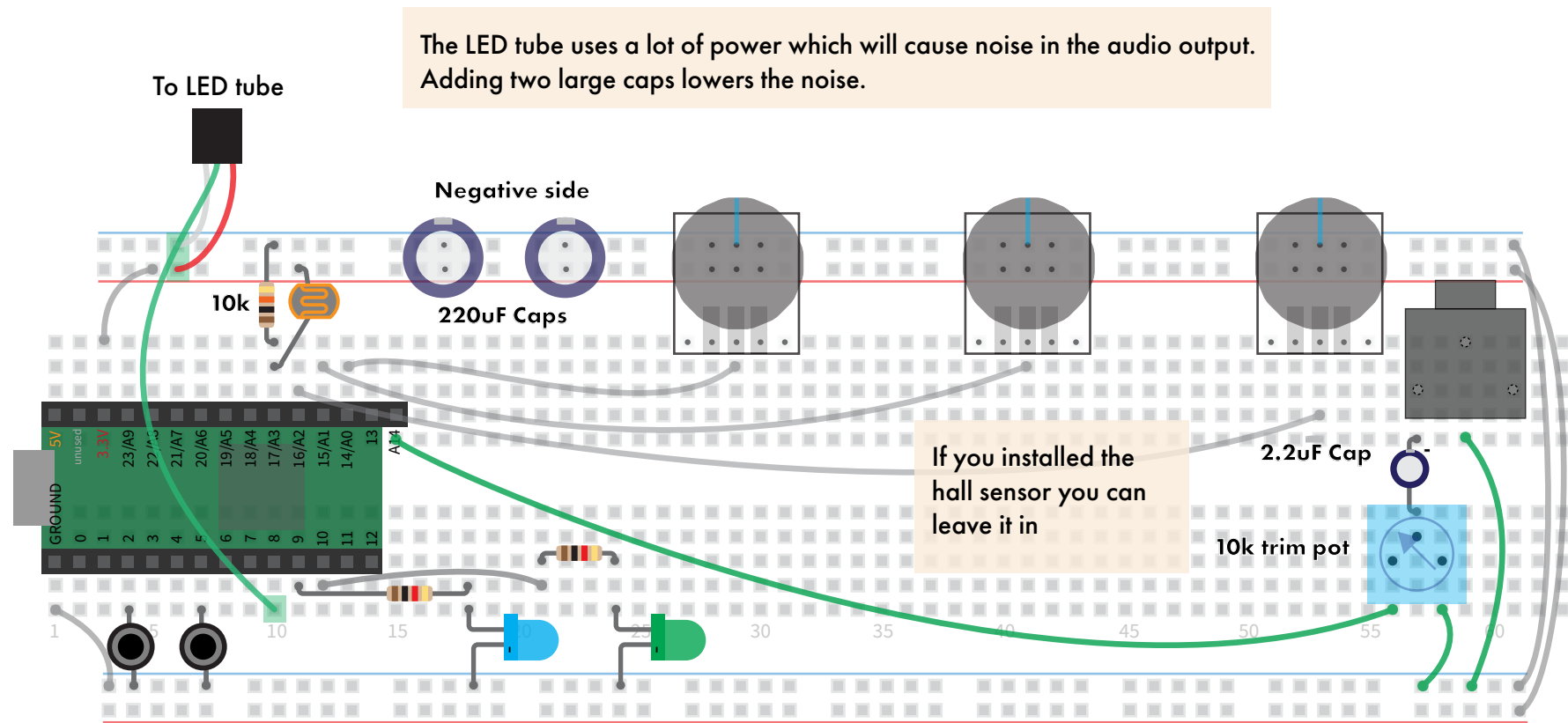


Breadboard setup #6 - Audio out

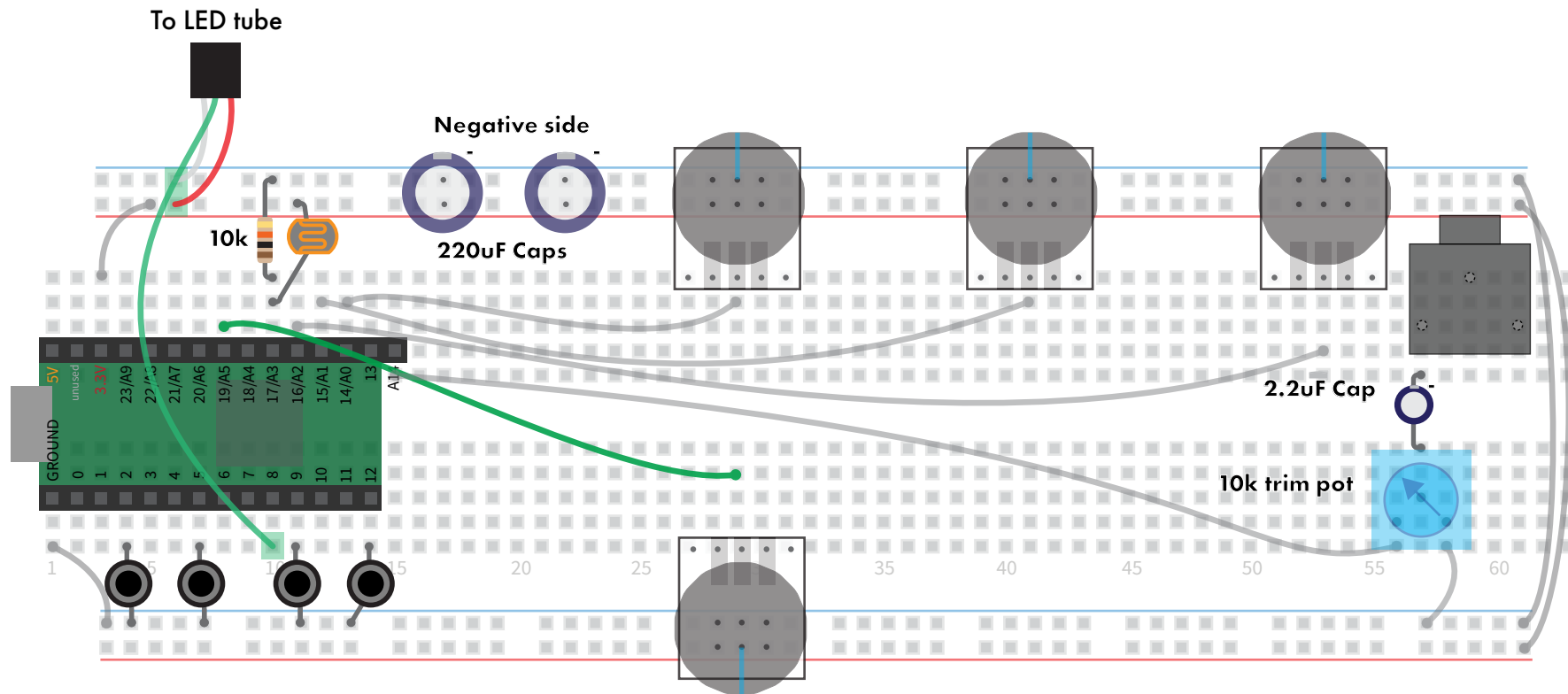

A14 is a 12bit DAC output. This produces real analog signals, not PWM. The blue pot is a volume control. The other pots can work this way too but this one saves space and is an example of how to use these tiny "trimmer" potentiometers. This as analog volume control. We could do it in the code but would loose bit depth.



The standard LEDs have been removed.
Two more buttons and another pot are installed.