

Breadboard setup class #8 - Servos

Servos can attach to any PWM pin. See the github page to see which those are. They need to be powered by 5V, not 3.3V. Be careful not to attach 5V to anything else as it can damage the Teensy.

The audio out, encoder, and other devices we've used aren't shown here to simplify the diagram. You can use them all at the same time.

